

**CBSE CLASS X**  
**Science (086)**

## QUESTION PAPER

AI-generated question paper

Code: IBDQC5

Questions: 31

Maximum Marks: 68

Generated: 2026-06-25 17:50

**SELECTIONS USED**

Subject	Science
Lessons	11 Electricity
Level of understanding	Exam-ready
Question selection	CBSE board paper, whole lesson (~80 marks across Sections A-E)
Model	claude-sonnet-4-6

Composition — Difficulty: 9 straightforward · 17 medium · 5 deep | Types: 10 MCQ · 6 Short · 5 Assertion–reason · 4 Very short · 3 Long · 3 Case-based | Sections: A 15Q/15m · B 4Q/8m · C 6Q/18m · D 3Q/15m · E 3Q/12m

**Q1.** straightforward exam-ready

[1]

The potential difference across a conductor is doubled while its resistance remains unchanged. The current through it will:

- (A) be halved
  - (B) remain the same
  - (C) be doubled
  - (D) become four times
- A be halved
  - B remain the same
  - C be doubled
  - D become four times

◆ Electricity

**Q2.** straightforward exam-ready

[1]

Which of the following correctly gives the SI unit of electrical resistivity?

- (A)  $\Omega$
  - (B)  $\Omega \text{ m}^{-1}$
  - (C)  $\Omega \text{ m}$
  - (D)  $\Omega \text{ m}^2$
- A  $\Omega$
  - B  $\Omega \text{ m}^{-1}$
  - C  $\Omega \text{ m}$
  - D  $\Omega \text{ m}^2$

◆ Electricity

**Q3.** medium exam-ready

[1]

A wire of resistance  $R$  is stretched uniformly until its length is doubled. Its new resistance will be:

- (A)  $R/2$
- (B)  $R$
- (C)  $2R$
- (D)  $4R$

- A  $R/2$
- B  $R$
- C  $2R$
- D  $4R$

◆ Electricity

**Q4.** straightforward exam-ready

[1]

Which term does NOT correctly represent electric power consumed in a circuit?

- (A)  $I^2R$
- (B)  $IR^2$
- (C)  $V^2/R$
- (D)  $VI$

- A  $I^2R$
- B  $IR^2$
- C  $V^2/R$
- D  $VI$

◆ Electricity

**Q5.** straightforward exam-ready

[1]

The commercial unit of electrical energy, 1 kWh, is equal to:

- (A) 1000 J
- (B)  $3.6 \times 10^4$  J
- (C)  $3.6 \times 10^6$  J
- (D)  $3.6 \times 10^8$  J

- A 1000 J
- B  $3.6 \times 10^3$  J
- C  $3.6 \times 10^6$  J
- D  $3.6 \times 10^4$  J

◆ Electricity

**Q6.** medium exam-ready

[1]

The heat produced in a conductor when current  $I$  flows through it for time  $t$  is  $H = I^2Rt$ . If the current is doubled and the time is halved, the heat produced will be:

- (A) remain the same
- (B) doubled
- (C) halved
- (D) quadrupled

- A remain the same
- B doubled
- C halved
- D quadrupled

◆ Electricity

**Q7.** medium exam-ready**[1]**

A 100 W electric bulb and a 40 W electric bulb are both designed for 220 V. Which bulb has higher resistance?

- (A) The 100 W bulb
- (B) The 40 W bulb
- (C) Both have the same resistance
- (D) Cannot be determined from given data

- A The 100 W bulb
- B The 40 W bulb
- C Both have the same resistance
- D Cannot be determined from given data

◆ Electricity

**Q8.** straightforward exam-ready**[1]**

The resistivity of a material depends on:

- (A) the length of the conductor
- (B) the area of cross-section of the conductor
- (C) the nature of the material and temperature
- (D) both the length and area of cross-section

- A the length of the conductor
- B the area of cross-section of the conductor
- C the nature of the material and temperature
- D both the length and area of cross-section

◆ Electricity

**Q9.** straightforward exam-ready**[1]**

The V–I graph for a metallic wire at constant temperature is a straight line passing through the origin. This is a graphical representation of:

- (A) Joule's law of heating
- (B) Ohm's law
- (C) Kirchhoff's voltage law
- (D) Faraday's law

- A Joule's law of heating
- B Ohm's law
- C Kirchhoff's voltage law
- D Faraday's law

◆ Electricity

**Q10.** medium exam-ready**[1]**

An electric motor operates at 220 V and draws a current of 5 A. The energy consumed by the motor in 1 hour is:

- (A) 1100 J
- (B)  $3.96 \times 10^3$  J
- (C)  $3.96 \times 10^6$  J
- (D)  $3.96 \times 10^4$  J

- A 220 J
- B 1100 J
- C  $3.96 \times 10^6$  J
- D 1100 W

◆ Electricity

**Q11.** medium exam-ready

[1]

Assertion (A): Alloys are preferred over pure metals for making the heating elements of electric irons and toasters.

Reason (R): Alloys have higher resistivity and do not oxidise easily at high temperatures.

- (A) Both A and R are true and R is the correct explanation of A.  
(B) Both A and R are true but R is not the correct explanation of A.  
(C) A is true but R is false.  
(D) A is false but R is true.

- A Both A and R are true and R is the correct explanation of A.  
B Both A and R are true but R is not the correct explanation of A.  
C A is true but R is false.  
D A is false but R is true.

## ◆ Electricity

**Q12.** medium exam-ready

[1]

Assertion (A): In a parallel combination of resistors, the equivalent resistance is always less than the smallest individual resistance in the combination.

Reason (R): Adding more parallel paths provides additional routes for current, effectively reducing total opposition to current flow.

- (A) Both A and R are true and R is the correct explanation of A.  
(B) Both A and R are true but R is not the correct explanation of A.  
(C) A is true but R is false.  
(D) A is false but R is true.

- A Both A and R are true and R is the correct explanation of A.  
B Both A and R are true but R is not the correct explanation of A.  
C A is true but R is false.  
D A is false but R is true.

## ◆ Electricity

**Q13.** straightforward exam-ready

[1]

Assertion (A): Tungsten is used for making filaments of electric bulbs.

Reason (R): Tungsten has a very high melting point (3380°C) and high resistivity, which allows it to become incandescent without melting.

- (A) Both A and R are true and R is the correct explanation of A.  
(B) Both A and R are true but R is not the correct explanation of A.  
(C) A is true but R is false.  
(D) A is false but R is true.

- A Both A and R are true and R is the correct explanation of A.  
B Both A and R are true but R is not the correct explanation of A.  
C A is true but R is false.  
D A is false but R is true.

## ◆ Electricity

**Q14.** straightforward exam-ready**[1]**

Assertion (A): The direction of conventional electric current in a metallic conductor is taken opposite to the direction of flow of electrons.

Reason (R): Electrons were not known when the phenomenon of electricity was first studied, so current was assumed to flow from positive to negative terminal.

- (A) Both A and R are true and R is the correct explanation of A.  
(B) Both A and R are true but R is not the correct explanation of A.  
(C) A is true but R is false.  
(D) A is false but R is true.

- A Both A and R are true and R is the correct explanation of A.  
B Both A and R are true but R is not the correct explanation of A.  
C A is true but R is false.  
D A is false but R is true.

## ◆ Electricity

**Q15.** medium exam-ready**[1]**

Assertion (A): The cord (connecting wire) of an electric heater does not glow, but its heating element does.

Reason (R): The heating element has much higher resistance than the cord, so it dissipates far more heat for the same current.

- (A) Both A and R are true and R is the correct explanation of A.  
(B) Both A and R are true but R is not the correct explanation of A.  
(C) A is true but R is false.  
(D) A is false but R is true.

- A Both A and R are true and R is the correct explanation of A.  
B Both A and R are true but R is not the correct explanation of A.  
C A is true but R is false.  
D A is false but R is true.

## ◆ Electricity

**Q16.** straightforward exam-ready**[2]**

Define electric potential difference between two points in a circuit. Write the formula relating it to work done and charge.

## ◆ Electricity

**Q17.** medium exam-ready**[2]**

A nichrome wire of length 2 m and cross-sectional area  $0.5 \text{ mm}^2$  has a resistance of  $4 \Omega$ . Calculate the resistivity of nichrome.

## ◆ Electricity

**Q18.** medium exam-ready**[2]**

An electric heater is rated 2 kW at 220 V. A fuse rated 5 A is installed in the circuit. Will the fuse operate safely? Justify your answer with a calculation.

## ◆ Electricity

**Q19.** deep exam-ready**[2]**

Two resistors of  $6 \Omega$  and  $3 \Omega$  are first connected in series and then in parallel across the same 12 V battery. Find the ratio of total power dissipated in the series arrangement to that in the parallel arrangement.

## ◆ Electricity

**Q20.** medium exam-ready [3]

Derive an expression for the equivalent resistance of three resistors  $R_1$ ,  $R_2$ , and  $R_3$  connected in series. Using this result, explain why the equivalent resistance in a series combination is always greater than any individual resistance in the combination.

◆ Electricity

**Q21.** medium exam-ready [3]

A battery of 15 V is connected to three resistors of 3  $\Omega$ , 4  $\Omega$ , and 8  $\Omega$  connected in parallel. Calculate: (a) the equivalent resistance of the combination, (b) the total current drawn from the battery, and (c) the current through the 8  $\Omega$  resistor.

◆ Electricity

**Q22.** medium exam-ready [3]

State Joule's law of heating. An electric iron of resistance 25  $\Omega$  is operated at 200 V for 30 minutes. Calculate the heat produced in the iron during this time.

◆ Electricity

**Q23.** medium exam-ready [3]

(a) State any two advantages of connecting electrical appliances in parallel rather than in series in a domestic circuit.  
(b) Three identical bulbs are connected in parallel across a 12 V source and the total current drawn is 3 A. Calculate the resistance of each bulb.

◆ Electricity

**Q24.** deep exam-ready [3]

Two wires X and Y are made of the same material. Wire X has twice the length and half the cross-sectional area of wire Y. Compare the resistances of X and Y. If both are connected in series to a 6 V battery, what fraction of the total voltage appears across wire Y?

◆ Electricity

**Q25.** medium exam-ready [3]

(a) Define electric power and write its SI unit.  
(b) A household uses the following appliances: one 1000 W electric iron for 2 hours, two 60 W fans for 5 hours, and one 100 W television for 4 hours every day. Calculate the total electrical energy consumed in one day in kWh.

◆ Electricity

**Q26.** deep exam-ready [5]

(i) Derive an expression for the equivalent resistance when three resistors  $R_1$ ,  $R_2$ , and  $R_3$  are connected in parallel. Mention one practical advantage of this combination over a series combination.  
(ii) The resistivities of copper and nichrome are  $1.62 \times 10^{-8} \Omega \text{ m}$  and  $100 \times 10^{-6} \Omega \text{ m}$  respectively. Both wires have the same length and the same cross-sectional area. Calculate the ratio of resistance of nichrome wire to copper wire. Which material would you prefer for making the element of an electric toaster, and why?

◆ Electricity

**Q27.** deep exam-ready**[5]**

- (i) State Joule's law of heating and derive the expression  $H = I^2Rt$ .
- (ii) An electric kettle of resistance  $44 \Omega$  is rated for  $220 \text{ V}$ . Calculate: (a) the current through the kettle, (b) the power consumed, and (c) the heat generated in 5 minutes of operation.
- (iii) Why is tungsten used for making filaments of electric bulbs rather than copper, even though copper is a better conductor?

◆ Electricity

**Q28.** deep exam-ready**[5]**

- (i) What factors affect the resistance of a metallic conductor? Write the mathematical relation showing how resistance depends on each factor, and define resistivity.
- (ii) A copper wire of diameter  $0.4 \text{ mm}$  and resistivity  $1.62 \times 10^{-8} \Omega \text{ m}$  is to be used as a resistor in a circuit requiring a resistance of  $10 \Omega$ . Calculate the length of wire needed.
- (iii) If this copper wire is replaced by an aluminium wire of the same length and diameter (resistivity of aluminium =  $2.63 \times 10^{-8} \Omega \text{ m}$ ), how does the resistance change?

◆ Electricity

**Q29.** medium exam-ready**[4]**

Read the following information and answer the questions that follow:

Meera sets up a circuit with a  $6 \text{ V}$  battery, an ammeter, a plug key, and three resistors of  $2 \Omega$ ,  $3 \Omega$ , and  $6 \Omega$  connected in parallel.

- (a) Calculate the equivalent resistance of the three resistors connected in parallel. [1 mark]
- (b) Calculate the total current shown by the ammeter. [1 mark]
- (c) Find the current flowing through the  $2 \Omega$  resistor alone. [1 mark]
- (d) If Meera disconnects the  $6 \Omega$  resistor from the parallel combination while keeping the other two connected, will the total current increase, decrease, or remain the same? Justify your answer in one sentence. [1 mark]

◆ Electricity

**Q30.** medium exam-ready**[4]**

Read the following information and answer the questions that follow:

A technician tests various conductors in a laboratory at constant temperature. She records that nichrome has a resistivity of  $100 \times 10^{-6} \Omega \text{ m}$ , while silver has a resistivity of  $1.60 \times 10^{-8} \Omega \text{ m}$ . She uses a nichrome wire of length  $1 \text{ m}$  and cross-sectional area  $1 \times 10^{-6} \text{ m}^2$  as a heating element.

- (a) The technician observes that for the conductor at constant temperature, the current is directly proportional to the potential difference applied. Which law does this represent? State the law. [1 mark]
- (b) Which material — nichrome or silver — is a better conductor of electricity? Justify your answer using the given data. [1 mark]
- (c) Calculate the resistance of the nichrome heating element. [1 mark]
- (d) If the cross-sectional area of the nichrome wire is doubled while its length remains the same, what will be the new resistance? [1 mark]

◆ Electricity

**Q31.** medium exam-ready**[4]**

Read the following information and answer the questions that follow:

A household has the following electrical appliances all connected in parallel to a 220 V mains supply: a 1100 W electric iron, a 100 W television, and a 60 W table fan. The household uses a single fuse in the main line to protect the circuit.

- (a) Calculate the total current drawn from the mains when all three appliances are operating simultaneously. [1 mark]
- (b) The family has fuses of ratings 5 A and 10 A available. Which fuse should be used in the main line, and why? [1 mark]
- (c) Explain briefly how a fuse wire protects the appliances in a circuit when excessive current flows. [1 mark]
- (d) If the electric iron is operated daily for 2 hours and the cost of electricity is ₹3.00 per kWh, what is the cost of running the iron for 30 days? [1 mark]

◆ Electricity

---

Available for free from:  
<https://cbsegrade10studyguide.com>  
<https://github.com/orgs/cbse-free-resources/repositories>